

Remi de Ferrieres
X664611
CS 120A Section 021
Lab 6 – Timer Design – Laser surgery system
Yann Abou Jaoude
X663581

OVERVIEW:

In the first part of this lab, we worked on the implementation of a flight attendant call system using Verilog. We use the FPGA board to visualize the results. There were two buttons, one for lighting up a led, the other one to turn it off, all this using a clock source (internal).

In the second part we worked on the implementation of an FSM developed on Verilog (rising edge detector). Using the FPGA board, we wanted to visualize a clock rising edge and falling edge (led on for rising and off for falling edge). The clock frequency was too important at first (25MHz) so we had to include a bit of code to reduce this frequency to be able to notice the led with our eyes.

In the third part of the lab we worked on LED display time multiplexing. Implementing in Verilog a circuit.

ANALYSIS:

RECORDS:


- Source Code Part1:

```
module Verilog_lab_4(  
    input wire clk,  
    input wire call_button ,  
    input wire cancel_button ,  
    output reg light_state );  
    reg c_state ;  
    // Combinatorial block  
    always @(*) begin  
        case ({call_button, cancel_button})  
            2'b00: c_state = light_state? 'd1:'d0;  
            2'b01: c_state='d0;  
            2'b10: c_state='d1;  
            2'b11: c_state='d1;  
            default : c_state = 'd0 ;  
        endcase  
    end  
    // Sequential block  
    always @( posedge clk ) begin  
        light_state <= c_state ;  
    end  
endmodule
```

- UCF file Part1:

```
// Inputs
NET "clk" LOC = "B8";
NET "call_button" LOC = "A7";
NET "cancel_button" LOC = "M4";
// Outputs
NET "light_state" LOC = "M11";
```

- Simulation/Wave Form:

 

- Source code Part2:

```

`timescale 1ns / 1ps
module Verilog_lab_4_2(
    input wire clk,
    input wire signall,
    output reg outedge
);

wire slow_clk ;

reg [1:0] c_state ;
reg [1:0] r_state ;

localparam ZERO = 'd0;
localparam CHANGE = 'd1;
localparam ONE = 'd2;
// http://www-inst.eecs.berkeley.edu/~cs150/sp12/agenda/lec/lec17-FSM.pdf
clkdiv cl(clk, slow_clk );

// Comb. logic.

always @(*) begin

    case (r_state)

        ZERO : begin
            c_state = signall ? CHANGE : ZERO ;
            outedge = 'd0 ;
        end

        CHANGE : begin
            c_state = signall ? ONE : ZERO ;
            outedge = 'd1 ;
        end

        ONE : begin
            c_state = signall ? ONE : ZERO ;
            outedge = 'd0 ;
        end

        default : begin
            c_state = ZERO ;
            outedge = 'd0 ;
        end

    endcase

end

// -----
// Seq. logic
// -----

always @( posedge slow_clk ) begin
    r_state <= c_state ;
end

endmodule

```

```

module clkdiv(clk,clk_out);

    input clk;
    output clk_out;

    reg [15:0] COUNT;

    assign clk_out=COUNT[15];

    always @(posedge clk)
    begin
        COUNT = COUNT + 1;
    end

endmodule

```

- UCF file Part2:

```

// Inputs
NET "clk" LOC = "B8";
NET "signall" LOC = "A7";
// Outputs
NET "outedge" LOC = "M5";

```

- Simulation/Wave Form part 2:



- Source code part 3:

```

1  module dispmux_main_bh(
2  input clk , // Clock signal
3  input sw0, // Switch input
4  input sw1, // Switch input
5  input sw2, // Switch input
6  input sw3, // Switch input
7  output [3:0] an , // LED selector
8  output [7:0] sseg // Segment signals
9  );
10 wire [7:0] in0; wire [7:0] in1; wire [7:0] in2; wire [7:0] in3;
11 // -----
12 // Module instantiation bcdto7led
13 // -----
14 bcdto7led_bh c1(sw0, sw1, sw2, sw3,
15 in0[0],in0[1],in0[2],in0[3], in0[4],in0[5],in0[6],in0[7] );
16
17 bcdto7led_bh c2(sw0, sw1, sw2, sw3,
18 in1[0],in1[1],in1[2],in1[3], in1[4],in1[5],in1[6],in1[7] );
19
20 bcdto7led_bh c3(sw0, sw1, sw2, sw3,
21 in2[0],in2[1],in2[2],in2[3], in2[4],in2[5],in2[6],in2[7] );
22
23 bcdto7led_bh c4(sw0, sw1, sw2, sw3,
24 in3[0],in3[1],in3[2],in3[3], in3[4],in3[5],in3[6],in3[7] );
25 // -----
26 // Module instantiation Mux
27 // -----
28 disp_mux_bh c5(
29 .clk (clk) ,
30 .in0 (in0) ,
31 .in1 (in1) ,
32 .in2 (in2) ,
33 .in3 (in3) ,
34 .an (an) ,
35 .sseg (sseg ) ) ;
36 endmodule
37
38 module bcdto7led_bh(
39 input wire sw0 , // Switches
40 input wire sw1 ,
41 input wire sw2 ,
42 input wire sw3 ,
43 output reg a , // LED segments
44 output reg b ,
45 output reg c ,
46 output reg d ,
47 output reg e ,
48 output reg f ,
49 output reg g ,
50 output reg h
51 );
52
53 // Internal wire
54 wire [3:0] bundle ;
55 assign bundle = {sw3,sw2,sw1,sw0 } ;
56 always @(*) begin
57
58 // Display in the module AN3
59 // Setting the segments signals
60 a = 1'b1 ;
61 b = 1'b1 ;
62 c = 1'b1 ;
63 d = 1'b1 ;
64 e = 1'b1 ;
65 f = 1'b1 ;
66 g = 1'b1 ;
67 h = 1'b1 ;
68
69 case ( bundle )
70 4'b0000 : begin // 0
71 a = 1'b0 ;
72 b = 1'b0 ;
73 c = 1'b0 ;
74 d = 1'b0 ;
75 e = 1'b0 ;
76 f = 1'b0 ;
77 end

```

The code continues with all the cases of each number display..

- UCF file part 3:

```

1  // Inputs
2  NET "clk" LOC = "B8";
3  NET "sw0" LOC = "A7";
4  NET "sw1" LOC = "M4";
5  NET "sw2" LOC = "C11";
6  NET "sw3" LOC = "G12";
7  // Outputs
8  NET "an[0]" LOC = "K14";
9  NET "an[1]" LOC = "M13";
10 NET "an[2]" LOC = "J12";
11 NET "an[3]" LOC = "F12";
12 NET "sseg[0]" LOC = "L14";
13 NET "sseg[1]" LOC = "H12";
14 NET "sseg[2]" LOC = "N14";
15 NET "sseg[3]" LOC = "N11";
16 NET "sseg[4]" LOC = "P12";
17 NET "sseg[5]" LOC = "L13";
18 NET "sseg[6]" LOC = "M12";

```

CONCLUSION:

The purpose of the lab is to introduce us to sequential logic. Although the result is very similar to the previous lab, the processing of information is quite different. In the previous lab we have seen combinatorial logic. All input arrived at the same time. From now on, we have an overview of the sequential logic: data entered at the input of the first flip-flop propagates in the following flip-flops to each signal of the clock.

DISCUSSION:

The system works. We thought we had a problem because the 4 digits were lit. The lab manual seemed to indicate that the result should be a simple hexadecimal counter. We thought only one digit would come on. That said, we did not want to change the piece of code given in manual. After a few attempts, the teacher told us that everything was normal. The only other problem is always to navigate the software. We often have to use the manual of previous labs.

To improve our system, we could:

- Make a 4-digit hexadecimal counter rather than having the same digit on the 4 displays.
- Increase the frequency of the clock, to make our system even more responsive.

QUESTIONS:

1. What will happen if the "clock" signal is of very low frequency (1 Hz)? There will have a big delay between the moment the button is pressed to the result. More precisely, we will have to wait until a rising edge. For a 1hz frequency, we may wait 0 to 1 sec.
2. Design a test-bench and verify the logic performance. We must test successively every input of the truth table. The results are seen on our waveform above.