Remi de Ferrieres X664611 CS 120A Section 021 Lab 6 – Timer Design – Laser surgery system Yann Abou Jaoude X663581

#### **OVERVIEW**

In this lab we worked on system of laser surgery. Especially around the timer. For testing the system, we had to change the timer in order to make it tick every 10s.

### **ANALYSIS**

#### Source code:

```
module VerilogLab6 # (
 parameter NBITS = 32
input wire b ,
input wire clk
output reg light
reg reset;
wire timer;
reg [1:0] current_state ;
reg [1:0] next_state ;
wire [NBITS-1:0] cnt_ini ;
wire [NBITS-1:0] cnt_rst ;
// Sequential logic
always @(posedge clk) begin
current_state = next_state ;
end
// -----
// Comb. Logic
assign cnt_ini = 32'h0000;
assign cnt_rst = 32'hEE6B280; // 10 secs ( 25 MHZ internal clock )
// Comb. Logic - FSM
localparam OFF = 2'b00;
localparam START = 2'b01;
localparam ON = 2'b10 ;
always @( current_state ) begin
case (current_state)
 OFF : begin
                                                                                    next_state = OFF;
 light = 1'b0 ;
 reset = 1'b1;
if(b == 1)
                                                                                 else begin
                                                                                   next_state = ON;
   begin
                                                                                 end
                                                                              end
      next_state = START;
                                                                              default: begin
                                                                             light = 1'b0;
reset = 1'b0;
    else begin
      next_state = OFF;
                                                                             next_state = OFF ;
    end
                                                                              end
                                                                             endcase
 START : begin
                                                                             // -----
 next_state = ON;
                                                                             // Timer instantiation
 light = 1'b0 ;
reset = 1'b0 ;
                                                                             \mbox{timer\_st } \# \mbox{(.NBITS(NBITS))} \mbox{) timerst (}
                                                                             .timer(timer),
                                                                              .clk(clk),
 ON : begin
                                                                             .reset(reset) ,
.cnt_ini(cnt_ini) ,
    light = 1'b1 ;
    reset = 1'b0 ;
                                                                              .cnt_rst(cnt_rst)
    if(timer == 1)
                                                                              endmodule
```

The rest of the source code was given in the lab pdf. Constraint file:

```
# clock pin for Basys Board
// Inputs
NET "clk" LOC = "B8";
//NET "reset" LOC = "A7";
NET "b" LOC = "M4";
// Outputs
NET "light" LOC = "G1";
```

## **DISCUSSION**

Our Laser Surgery System worked just as specified in the lab manual. The light turned on during ten seconds and then turned off.

We had some trouble with the timer design. We thought we had to do it without help and we got lost when creating the module We have been unlocked on this part thanks to the next part.

## **CONCLUSION**

The purpose of this lab is to develop a structural verilog implementation of a system. Firstly, we programed a timer, witch is may be useful in almost every project. But through this example, we especially improved our ability to handle program pieces and verilog modules.

# **QUESTIONS**

There is no question in this Lab manual